

Implement a decimal to BCD encoder using 2-Input NAND gates

BCD stands for binary coded decimal and decimal is the number system with base 10. We have to implement a circuit with two input NAND gates to encode decimal to BCD.

Table of BCD code for 10 digits (0-9)

Decimal Digit	Binary Coded Decimal			
D	A	B	C	D
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

From the table we can see,


$$A = D_8 + D_9 \quad ('+' \text{ stands for 'OR'})$$

$$B = D_4 + D_5 + D_6 + D_7$$

$$C = D_2 + D_3 + D_6 + D_7$$

$$D = D_1 + D_3 + D_5 + D_7 + D_9$$

Teacher's Signature

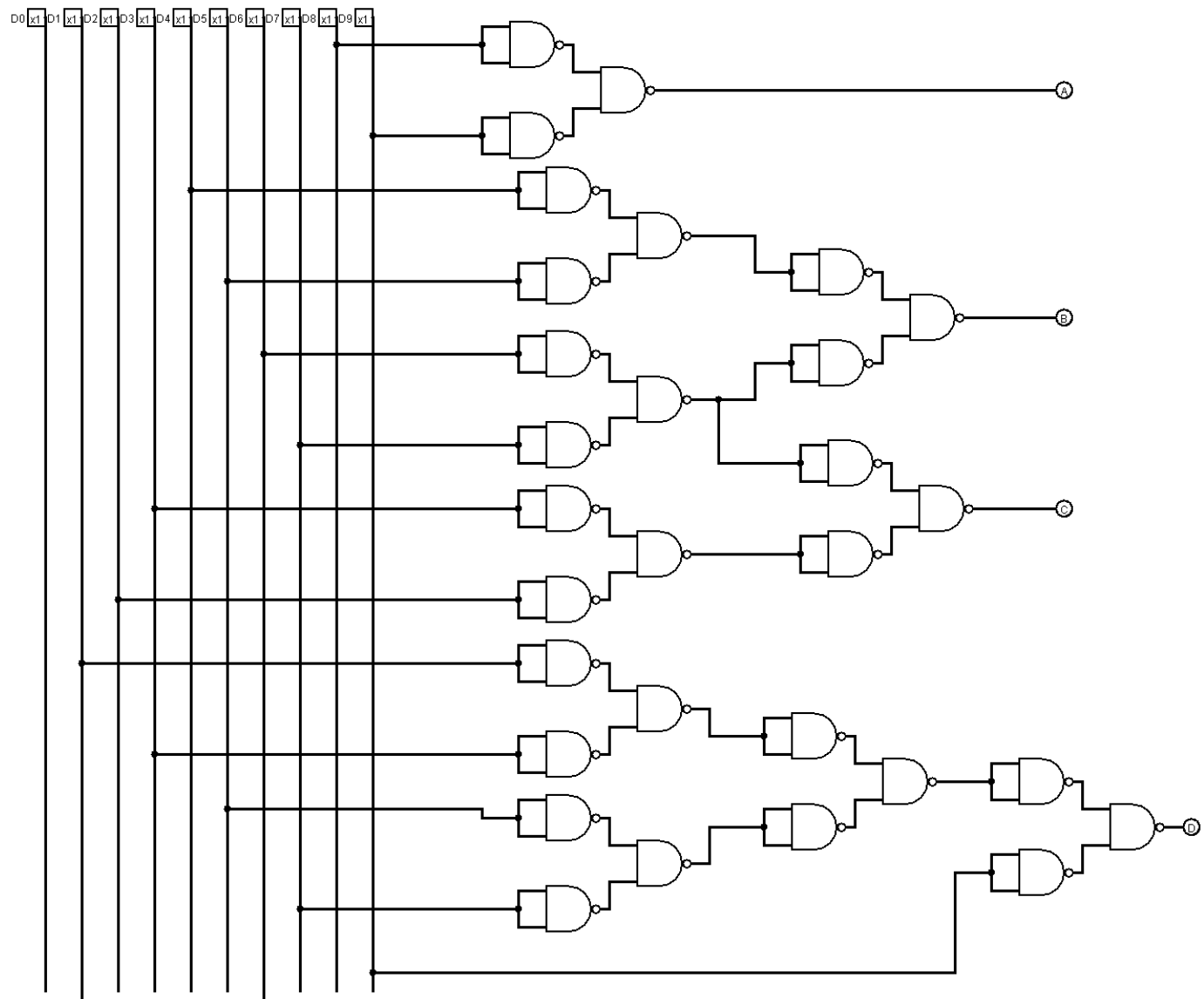

DECIMAL TO BCD ENCODER

Implement a BCD to decimal decoder using two input NAND gates.

Table of decimal digits with BCD code:

Binary Coded Decimal				Decimal Digit.
A	B	C	D	D
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9

from the Table we can see,

$$D_0 = \bar{A}\bar{B}\bar{C}\bar{D}$$

$$D_6 = \bar{A}B\bar{C}\bar{D}$$

$$D_1 = \bar{A}\bar{B}\bar{C}D$$

$$D_7 = \bar{A}B\bar{C}D$$

$$D_2 = \bar{A}\bar{B}C\bar{D}$$


$$D_8 = A\bar{B}\bar{C}\bar{D}$$

$$D_3 = \bar{A}\bar{B}CD$$

$$D_9 = A\bar{B}\bar{C}D$$

$$D_4 = \bar{A}B\bar{C}\bar{D}$$

$$D_5 = \bar{A}B\bar{C}D$$

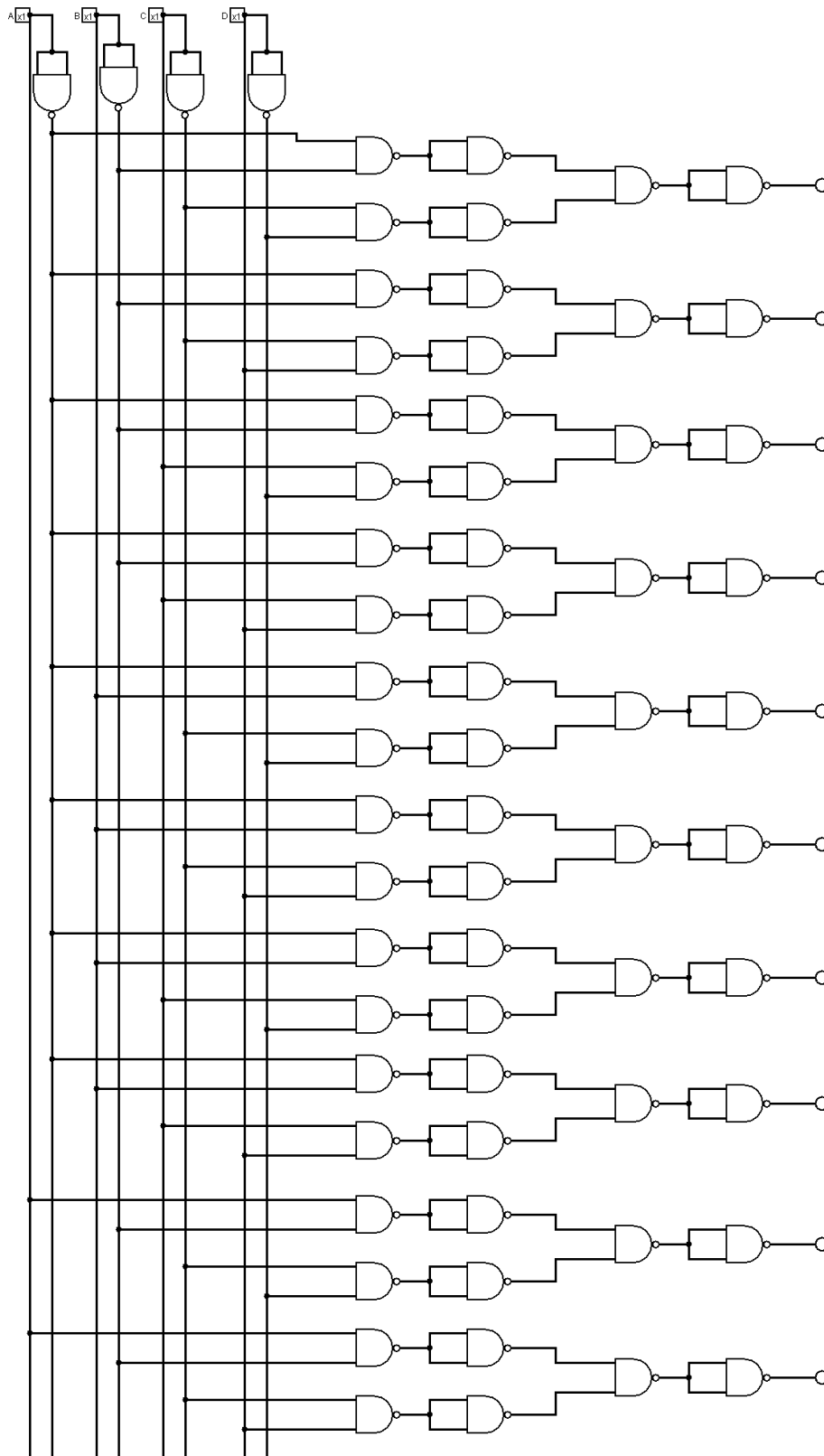

BCD TO DECIMAL DECODER