

Implement a comparator circuit for two 3-bit numbers using only 2-input NAND gates.

Name :- Imon Ray

Roll :- 002010501098

Dept :- CSE

What Is A Comparator Circuit?


A comparator circuit is used ~~to~~ to compare magnitude of two n-bit binary numbers.

Here, we will implement a 3-bit comparator circuit

Let, the two 3-bit numbers are A and B

There will be three possibilities \Rightarrow 1) $A=B$, 2) $A>B$, 3) $A<B$

$A = A_2 A_1 A_0$ and $B = B_2 B_1 B_0$

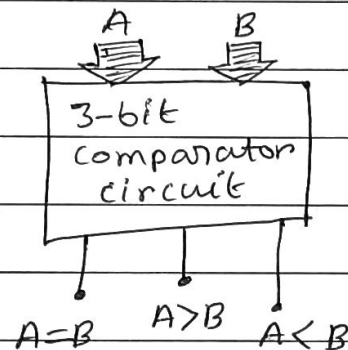

For $A=B$

In this case, corresponding bits will be equal

$$\therefore A_2 = B_2 \text{ and } A_1 = B_1 \text{ and } A_0 = B_0$$

● We can use XNOR to implement equality of bits

Here,

$$(\text{Output}) = (A_2 \odot B_2) \cdot (A_1 \odot B_1) \cdot (A_0 \odot B_0)$$

$$\text{output} = (\bar{A}_2 \bar{B}_2 + A_2 B_2) \cdot (\bar{A}_1 \bar{B}_1 + A_1 B_1) \cdot (\bar{A}_0 \bar{B}_0 + A_0 B_0)$$

For $A > B$

Case I: \rightarrow If $A_2 > B_2$

$$\Rightarrow A_2 = 1 \text{ and } B_2 = 0 \Rightarrow \text{Output} = A_2 \bar{B}_2$$

(other bit values doesn't matter)

Case II: \rightarrow

If $A_2 = B_2$ and $A_1 > B_1$,

$$\Rightarrow (A_2 \odot B_2) = 1 \text{ and } A_1 = 1 \text{ and } B_1 = 0$$

$$\text{output} \Rightarrow A_1 \bar{B}_1 (\bar{A}_2 \bar{B}_2 + A_2 B_2)$$

Case III: \rightarrow

If $A_2 = B_2$ and $A_1 = B_1$ and $A_0 > B_0$

$$\therefore \text{output} = A_0 \bar{B}_0 (\bar{A}_1 \bar{B}_1 + A_1 B_1) (\bar{A}_2 \bar{B}_2 + A_2 B_2)$$

So, Final Output for $A > B$

$$= A_2 \bar{B}_2 + A_1 \bar{B}_1 (\bar{A}_2 \bar{B}_2 + A_2 B_2) + A_0 \bar{B}_0 (\bar{A}_1 \bar{B}_1 + A_1 B_1) (\bar{A}_2 \bar{B}_2 + A_2 B_2)$$

For $A < B$

Case I: \rightarrow If $A_2 < B_2$

$$\therefore \text{output} = \bar{A}_2 B_2$$

Case II: \rightarrow

If $A_2 = B_2$ and $A_1 < B_1$,

$$\text{output} = \bar{A}_1 B_1 (\bar{A}_2 \bar{B}_2 + A_2 B_2)$$


Case II : \rightarrow If $A_2=B_2$ and $A_1=B_1$ and $A_0 < B_0$

$$\text{output} = \bar{A}_0 B_0 (\bar{A}_2 \bar{B}_2 + A_2 B_2) (\bar{A}_1 \bar{B}_1 + A_1 B_1)$$

Final output for $(A < B)$

$$= \bar{A}_2 B_2 + \bar{A}_1 B_1 (\bar{A}_2 \bar{B}_2 + A_2 B_2) + \bar{A}_0 B_0 (\bar{A}_2 \bar{B}_2 + A_2 B_2) (\bar{A}_1 \bar{B}_1 + A_1 B_1)$$

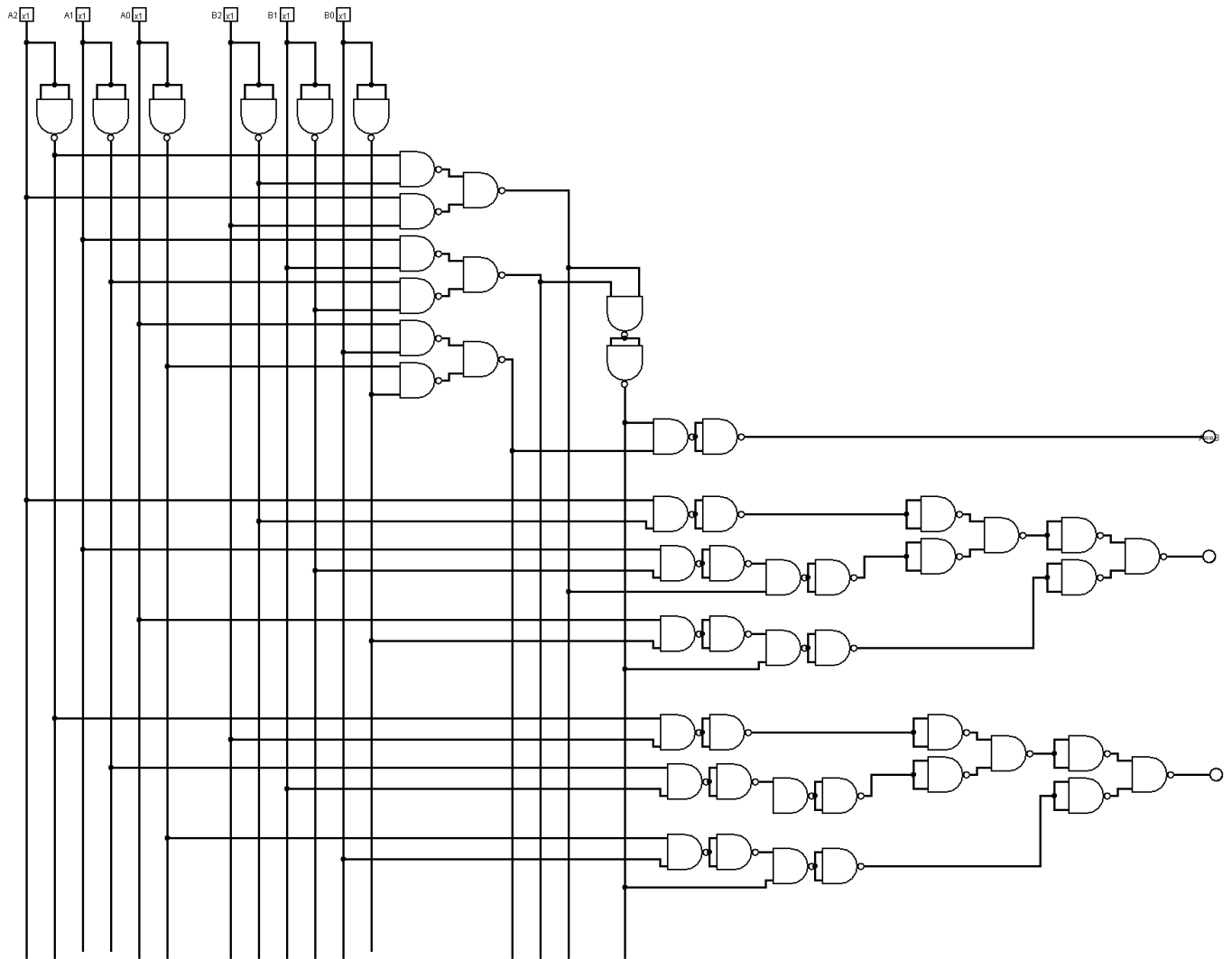Now, I will implement the circuit using only two input NAND gates.



FIRST OUTPUT: $A=B$ | SECOND OUTPUT: $A>B$

THIRD OUTPUT: $A<B$

THREE BIT COMPARATOR CIRCUIT