

Assignment 9: Design a 4-bit Ripple Up/Down counter (Asynchronous)

Ripple counter is a special type of Asynchronous Counter in which clock pulse ripples through the circuit.

Up counter counts the states in ascending order and down counter counts in descending order.

Up-Down counter is a bi-directional counter which counts in both direction (asc and desc).

We will use J-K flip-flops to implement the up-down counter.

As we will have to implement both up and down counter in same circuit we will have an input M .

If $M=0$ we will take it as ~~($M=0$)~~ up counter and if $M=1$ will act as down counter.

As here, the output of first flip-flop is given as clock to second flip-flop. Let's control using M to up or down.

● $M=0 \rightarrow Q$ is connected to next clock

● $M=1 \rightarrow \bar{Q}$ is connected to next clock

▣ NOW, the truth table for Y which will go to next clock.

M	Q	\bar{Q}	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

K-Map

M \ Q \bar{Q}	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$Y = \bar{M}Q + M\bar{Q} = M \oplus Q$$

Now we will implement the circuit, using J-K flip-flops and NAND gates.

4- Bit UP-down ripple counter circuit.

